

CS232 Week3 Q2

Vedang Dhirendra Asgaonkar 200050154

January 2022

1 Design of Four Bit Ripple Adder

For each position in the sum, we add together the corresponding positions from a, b and the carry from the previous addition using the one bit full adder.

$$sum(0), carry(0) = \text{OneBitFullAdd}(a(0), b(0), cin)$$

$$sum(1), carry(1) = \text{OneBitFullAdd}(a(1), b(1), carry(0))$$

$$sum(2), carry(2) = \text{OneBitFullAdd}(a(2), b(2), carry(1))$$

$$sum(3), cout = \text{OneBitFullAdd}(a(3), b(3), carry(2))$$