

# CS232 Week2 Q1

Vedang Dhirendra Asgaonkar (200050154)

January 2022

## 1 Design

### 1.1 MUX Design

The MUX has three input ports  $x_0, x_1, s$  and one output port  $o$ . It uses  $s$  as a switch on the inputs. In terms of Boolean algebra, it is implemented as

$$o = (x_1 \cdot s) + (x_0 \cdot \bar{s})$$

### 1.2 Encoder design

We convert each of the three outputs into its Reduced Ordered Binary Decision Diagram (ROBDD). Every node of the ROBDD can be converted into a MUX with the corresponding variable as its signal  $s$ . The port  $x_0$  of the MUX will receive the signal from the negative side of the node and  $x_1$  from the positive side. The enabler can be finally connected to the  $s$  of a MUX, taking  $x_0$  connected to **0** and  $x_1$  to the output for each output. We construct the circuit as follows

$$z_0 = i_1 + i_3 + i_5 + i_7$$

$$z_0 = M(\mathbf{0}, M(M(M(M(\mathbf{0}, \mathbf{1}, i_1), \mathbf{1}, i_3), \mathbf{1}, i_5), \mathbf{1}, i_7), en)$$

$$z_1 = i_2 + i_3 + i_6 + i_7$$

$$z_1 = M(\mathbf{0}, M(M(M(M(\mathbf{0}, \mathbf{1}, i_2), \mathbf{1}, i_3), \mathbf{1}, i_6), \mathbf{1}, i_7), en)$$

$$z_2 = i_4 + i_5 + i_6 + i_7$$

$$z_2 = M(\mathbf{0}, M(M(M(M(\mathbf{0}, \mathbf{1}, i_4), \mathbf{1}, i_5), \mathbf{1}, i_6), \mathbf{1}, i_7), en)$$

where, for MUX

$$o = M(x_0, x_1, s)$$