

CS232 Week3 Q3

Vedang Dhirendra Asgaonkar 200050154

January 2022

1 Design of Four Bit Adder/Subtractor

In case of subtraction, we note the following:

$$\begin{aligned}a - b & \text{ mod } 2^n \\&= a - b + 2^n \text{ mod } 2^n \\&= a + (2^n - 1 - b) + 1 \text{ mod } 2^n \\&= a + \bar{b} + 1 \text{ mod } 2^n \quad (*)\end{aligned}$$

where \bar{b} is produced by inverting all bits of b . Thus for addition, we consider a signal $b_2 = b$ and for subtraction $b_2 = \bar{b}$. Thus,

$$b_2(i) = b(i) \oplus cin \quad \forall i$$

Now, we add b_2 and a using the Four Bit Ripple Adder, taking the carry bit as 0 for addition and 1 for subtraction, thus accounting for the +1 in (*).

$$sum, cout = \text{FourBitRippleAdder}(a, b, cin)$$